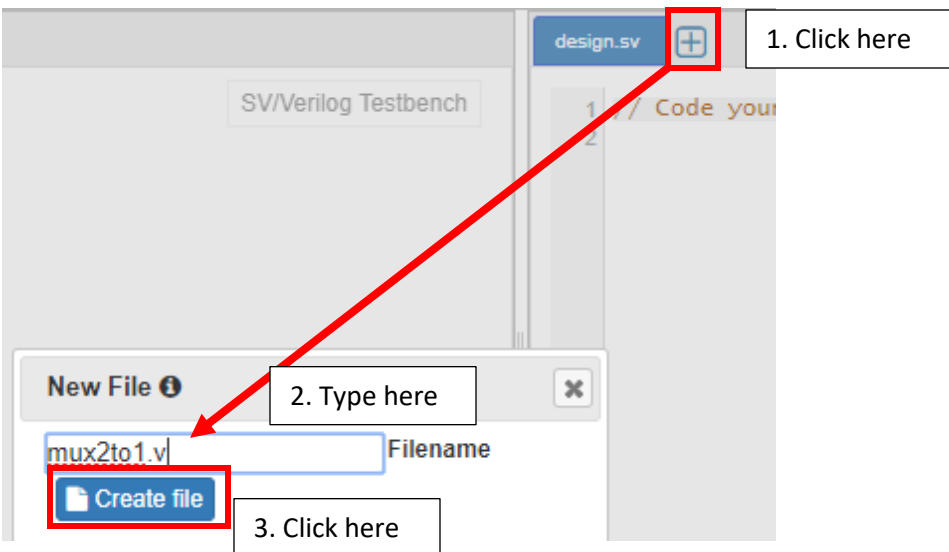


CECS 225: MUX TREE LAB

OBJECTIVE: Create a **4 to 1 mux** using multiple **2 to 1 multiplexers**

PROCEDURE: In a new project space on EDA playground, create a new source file named mux2to1.v




Create a module skeleton for your mux 2 to 1 using the exact same module name, input variables, and output variable as shown in the image below.



```
1 module mux2to1(input d0, d1, s,  
2                 output y);  
3  
4  
5 endmodule  
6
```


Use image below to complete the module skeleton and make a 2 to 1 multiplexer.

 

CECS 225: MUX TREE LAB

The design.sv file will contain what is known as your top level module. In hierarchical design, the module that connects together all other modules will be known as the top level module.

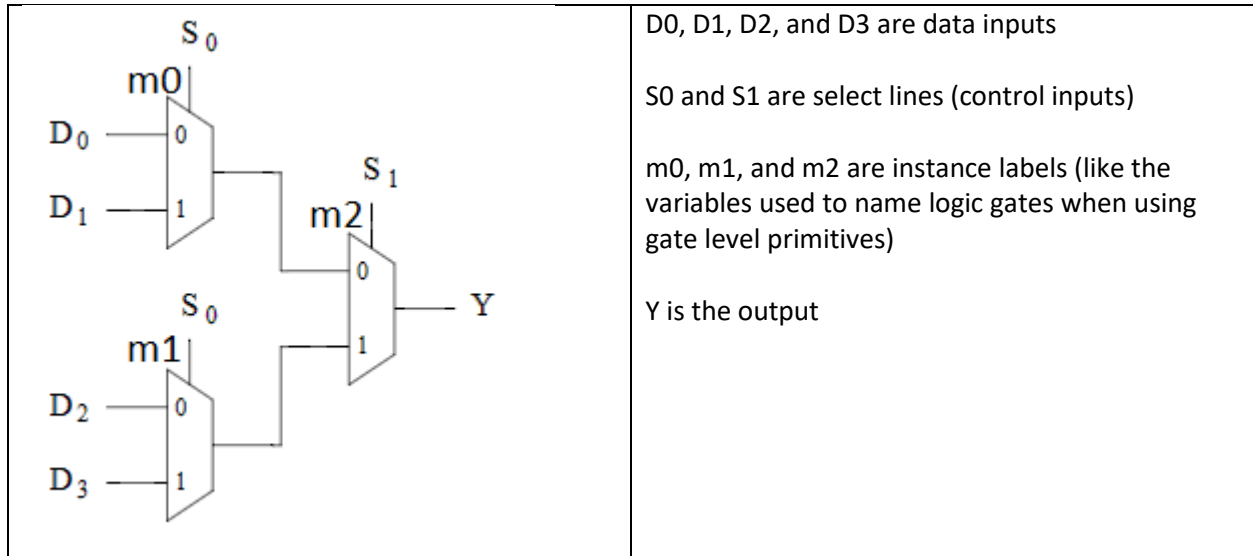Create a top level module which interconnects multiple instances of the mux2to1 according to the block diagram below:



Use the following module skeleton to get started:

```
`include "mux2to1.v"    //import mux2to1
module mux4to1(input d3,d2,d1,d0,s1,s0,
                output y);
    wire mux1out, mux0out;

    mux2to1
    m0(          ), //1st mux2to1 instance
    m1(          ), //2nd mux2to1 instance
    m2(          ); //3rd mux2to1 instance
endmodule
```

Pass variables into the port list parameter positions where the order of parameters must match the definition of the mux2to1 module.

Once you have modeled the circuit, its proper functionality can be verified using the tester on the following page.

CECS 225: MUX TREE LAB

SV/Verilog Testbe

```

1 module mux4to1tester;
2     reg d3,d2,d1,d0,s1,s0;
3     wire y;
4
5     mux4to1 dut(d3,d2,d1,d0,s1,s0,y);
6     integer i;
7     initial begin
8         $display("Mux 4 to 1 tester!");
9         d0 = 1'b1;    d1 = 1'b0;
10        d2 = 1'bx;    d3 = 1'b1;
11        $display("\tTest case\t d3\t d2\t d1\t d0\t\t s1\t s0\t\t ty");
12        for(i = 0; i < 4; i = i + 1)
13            begin
14                {s1,s0}=i;
15                #1 $display("%d\t\t %b\t %b\t %b\t %b\t\t\t %b\t %b\t\t %b", i, d3, d2, d1, d0, s1, s0, y);
16            end
17        $finish;
18    end
19 endmodule

```

Correct test results will appear as follows:

```
[2017-09-26 00:51:39 EDT] iverilog '-Wall' design.sv testbench.sv && unbuffer vvp a.out
```

Mux 4 to 1 tester!

Test case	d3	d2	d1	d0	s1	s0	y
0	1	x	0	1	0	0	1
1	1	x	0	1	0	1	0
2	1	x	0	1	1	0	x
3	1	x	0	1	1	1	1

Done

WHAT TO TURN IN: Once your mux4to1 module is completed and proper test results are produced:

- Copy the contents of your **mux4to1** module to a file named **mux4to1.txt**
- Upload **mux4to1.txt** to the beachboard dropbox for **mux4to1 lab**