 


## CECS 225: 8-BIT ARITHMETIC LOGIC UNIT

**OBJECTIVE:** Create an 8-bit ALU (Arithmetic Logic Unit).

**PROCEDURE:** First import the halfadder, fulladder, ripplecarry4, ripplecarry8, and ripplesubtractor8 module source files from the previous lab. *Be sure to use the exact same file names that were specified in the previous lab.*

Now create an 8-bit AND gate according to the block diagram below:




Name the file **and8.v** and use the module skeleton below to get started:

```
1 module and8(input [7:0] a,b,
2             output [7:0] y);
3     and
4     a0(y[0],a[0],    ),
5     a1(y[1],a[1],    ),
6     a2(y[2],a[ ],    ),
7     a3(y[3],a[ ],    ),
8     a4(y[4],        ,b[ ]),
9     a5(y[5],        ,b[ ]),
10    a6(y[6],        ,b[6]),
11    a7(y[7],        ,b[7]);
12 endmodule
```
 
## CECS 225: 8-BIT ARITHMETIC LOGIC UNIT

Then create an 8-bit OR gate according to the block diagram below:



Create a file named **or8.v** and use the skeleton code below to get started:

```
1 module or8(input [7:0] a,b,  
2             output [7:0] y);  
3     or  
4     o0(  
5     o1(  
6     o2(  
7     o3(  
8     o4(  
9     o5(  
10    o6(  
11    o7(  
12 endmodule
```

## CECS 225: 8-BIT ARITHMETIC LOGIC UNIT

The next two modules will be given for you to use:

Create **slt8.v** given the Verilog source code below:


```
1 module slt8(input [7:0] a,b,  
2             output reg [7:0] y);  
3     always @(*)  
4     begin  
5         if(a < b) y = 8'b0000_0001;  
6         else y = 8'b0000_0000;  
7     end  
8 endmodule
```

Create **mux8to1\_8bit.v** given the Verilog source code below:

```
1 module mux8to1_8bit(input [7:0] d0,d1,d2,d3,d4,d5,d6,d7,  
2                     input [2:0] s,  
3                     output reg [7:0] y);  
4     always @(*) begin  
5         case(s) //begin  
6             3'b000: y=d0;  
7             3'b001: y=d1;  
8             3'b010: y=d2;  
9             3'b011: y=d3;  
10            3'b100: y=d4;  
11            3'b101: y=d5;  
12            3'b110: y=d6;  
13            3'b111: y=d7;  
14            default: y=8'bx; //invalid output by default  
15        endcase  
16    end  
17 endmodule
```
 
## CECS 225: 8-BIT ARITHMETIC LOGIC UNIT

Create the Arithmetic Logic Unit! Block diagram below:



Name your Verilog source file as **alu8.v**, a skeleton is shown below:

```
'include "mux8to1_8bit.v"
'include "slt8.v"
'include "or8.v"
'include "and8.v"
'include "ripplesubtractor8.v"
'include "ripplecarry8.v"

module alu8(input [2:0] funct_sel,
            input [7:0] a,b,
            output zero_flag,
            output [7:0] result);
    wire [7:0] andab, orab, addab, subab, sltab;

    and8 and8bit(a,b,      );
    or8 or8bit(a, ,orab);
    RippleCarry8 rc8(      ,a, b, addab,);
    RippleSubtractor8 rs8(funct_sel[2], , , subab,);
    slt8 slt8bit( , ,sltab);
    mux8to1_8bit m8(andab, , ,8'bx,8'bx,8'bx, ,sltab,
                    funct_sel,result);

    nor nor8(zero_flag, result[0], result[ ],      , result[3],
             result[4], result[ ], result[6],      );
endmodule
```

## CECS 225: 8-BIT ARITHMETIC LOGIC UNIT

Leave the **design.sv** file empty as we will not be using it in this project.

Source code for testbench.sv is provided below:

```
1  `include "alu8.v"
2  module alutester;
3      reg [7:0] a,b;  reg [2:0] funct_sel;
4      wire [7:0] result;  wire zero;
5      integer i;
6
7      alu8 uut(funct_sel,a,b,zero,result);
8
9      initial begin
10         b=8'b00001111; a=8'b01011010;
11         for(i = 0; i < 8; i = i + 1) begin
12             funct_sel=i; test_case;
13         end
14         a=8'b00001111; b=8'b01011010; i = i - 1;
15         test_case;  //one more test case!
16         $finish;
17     end
18
19     task test_case;
20     begin
21         #1;
22         case(i)
23             3'b000:  $display("\nTesting the AND function");
24             3'b001:  $display("\nTesting the OR function");
25             3'b010:  $display("\nTesting Addition");
26             3'b110:  $display("\nTesting Subtraction");
27             3'b111:  $display("\nTesting Set Less Than Function");
28             default: $display("\nInvalid Function Select Code!");
29         endcase
30         if(i == 2) i = 5;
31         $display("a = %b, b = %b, result = %b, zero=%b",a,b,result,zero);
32     end
33 endtask
34 endmodule
```

SV/Verilog Testbe

## CECS 225: 8-BIT ARITHMETIC LOGIC UNIT

If everything works correctly then the following console output will be produced:

Testing the AND function

a = 01011010, b = 00001111, result = 00001010, zero=0

Testing the OR function

a = 01011010, b = 00001111, result = 01011111, zero=0

Testing Addition

a = 01011010, b = 00001111, result = 01101001, zero=0

Testing Subtraction

a = 01011010, b = 00001111, result = 01001011, zero=0

Testing Set Less Than Function

a = 01011010, b = 00001111, result = 00000000, zero=1

Testing Set Less Than Function

a = 00001111, b = 01011010, result = 00000001, zero=0

## CECS 225: 8-BIT ARITHMETIC LOGIC UNIT

If your module did not work correctly get assistance from the instructor or a reputable student to troubleshoot your design.

**WHAT TO TURN IN:** Once the modules in this lab are working correctly:

- Copy the contents of your **alu8.v** module to a file named **alu8.txt**
- upload **alu8.txt** to the beachboard dropbox for **alu8**

**NOTE:**

Keep the source files from this lab as they will be used in future Labs!